# Design and Construction of a Stabilize Variable Power Supply Unit

Adelakun Adedayo Oke<sup>1\*</sup>, Rabiu Jamiu. Ariyo<sup>1</sup>, Egunjobi Abiodun Isiaka<sup>2</sup> Akinnubi Rufus Timotheu<sup>3</sup> 1.Department of Physical and Earth Sciences, Wesley University of Science and Technology, Ondo, Ondo State Nigeria

> 2.Department of Physics, Moshood Abiola Polytechnic, Abeokuta, Ogun State, Nigeria 3.Department of Physics, Adeyemi College Of Education, Ondo State, Nigeria Corresponding author : d\_onescientist@yahoo.com

### Abstract

The main objective of this work is to design and construct a stabilize variable power supply unit with a voltage range of 0.20v - 15.85v and current range of 0 - 3 Amps (45W) with a very low output impedance of 0.008 ohms. We also study the regulation characteristics of a constructed power supply units to a certain load and line regulation so as to determine its stability by comparing it to a standard power supply unit. Test and analysis were carried out using the constructed power supply unit to power loads (Rheostat) of 1260hms 1A and 110hms 4A. The major components used include transistors, regulator LM317.The output measurements showed that the power supply was functional and the measured values gave minima variation from the nominal designed values. The developed output power supply is much useful in measurements, laboratory works and general applications requiring power supply.

Keywords: variable power supply unit, impedance, line regulation

### **1.0 INTRODUCTION**

With today's technological advancement, new miniaturized electrical and electronic products continue to emerge and these products require either a very low AC source or DC source for their operation[1]. Many of the existing power supply devices with various levels of complexities and sophistication can only give a single DC output which cannot serve the same purpose when a very low AC power output is greatly desired. Hence, the need for designing and developing an output power supply that can serve a dual purpose of providing DC and AC outputs of different values for use in miniaturized electrical and electronic appliances as well as for various domestic and laboratory experimental purposes[1,3,9,6,10,11]. Power supply unit is a fundamental unit in electronics systems, which produces a dc output voltage to the system. The simplest form of power supply is the unregulated power supply which produces a ripple dc output. The use of regulators with the unregulated power supply produces a very smooth dc. These kinds of power supply are termed regulated power supply[5,7,13].

The construction of stabilize variable power supply unit in the department was prompted by unavailability, and deficiency of the available one which is required for experiments most especially physics and electronic experiments. The history of power supply to electronics has caused much attention to scientist and electrical/electronic engineers on the design and construction of regulated power supply.

Power supply has gone through modification over the years until the arrival of a unit to meet consumers' satisfaction. In 1967, the S. G. S Fairchild designs a dual power supply using the zener diode and Darlington transistor as stabilizers[7] [Fair Child Groups; 1967].

In 1973, H. Olsen, design a second generation integrated circuit (IC) voltage regulator that operate between the range of 5volts at 20MA or 7 - 20volts at 100MA [13].

G. L. Tater in 1976[8], design a power supply using the MPC 1000 super regulator for 15v at 10A. He used two Motorola positive voltage regulator each having a separate 18v - 24v secondary winding of the transformer[Tater; 1976]. Capability of the overall packaged optoelectronic system, consisting of the optical fiber, silicon mirror, CMOS photodiode, and the dc/dc converter, is demonstrated by generation of an electrical power of 60  $\mu$ W [2].

# 2.0 DESIGN PROCEDURE

The design (Fig.1) of the complete power supply is best understood by analyzing the various stages that constitute the system. The stages involved are the unregulated, the regulated, the gain control, the current amplifier, and the current limiter.

#### 2.1 THE UNREGULATED UNIT

With the use of a 220v-250v transformer, the a.c mains of 220v, 50Hz is step down to a 25Vr.m.s, by the transformer, which is suitable for the system. A bridge rectifier with four power diodes (IN4001) produces a full rectification of a 25Vr.m.s a.c voltage from the transformer to a d.c with an a.c component (ripple).

The rectified ripple voltage is further smoothened with the use of a capacitor ( $4700\mu$ F, 50v), which reduces this ripple. This unregulated voltage is gotten from the circuit (Fig.2) below. The reduce ripple voltage have a mean

www.iiste.org IISIE

d.c output given by:

 $\frac{1}{2}\nabla v = v_p - v_{d.c}$ and  $v = \frac{1}{4}fc$  for full-wave rectification. Hence,  $v_{d.c} = v_p - \frac{1}{4}fc$ , where  $v_p = v_{r.m.s} \times \sqrt{2} = 30 \times 1.4 = 10$ 

42V.

With a ripple of  $0.05875V_{,}$ 

 $v_{d.c} = 42V - \frac{1}{4} \times 50 \times 4700 \times 10^{-6} = 42 - 0.05875 = 41.94$ 

2.2 THE REGUALATED UNIT AND GAIN CONTROL UNIT

These units stabilize and control the variation of the output voltage within the specified voltage range as shown in figure below. The IC LM317 stabilizes the output voltage to a very stable one. The LM317 has know ground terminal, it adjust  $v_{out}$  to maintain a constant of 1.25v from the output terminal to the adjusted terminal. The regulator puts 1.25v across R<sub>1</sub>, so 70mA flows through it. The adjustment terminal draws very little current (50–100A). The output voltage does not depend on the input voltage and it is given by  $v_{out=1.25(1+\frac{R_2v}{R_1})volts}$ 

Since R<sub>2</sub> and R<sub>v</sub> are connected in parallel they act as one resistor with resultant resistance given by  $R_T = \frac{R_2 R_V}{R_2 + R_V} = \frac{4.2 \times 10^3 \times 5 \times 10^3}{4.2 \times 10^3 + 510^3} = \frac{2.1 \times 10^7}{9.2 \times 10^3} = 2.82K$ 

$$V_{OUT} = 1.25 \left( 1 + \frac{R_{2V}}{R_1} \right) = 1.25 \left( 1 + \frac{2.82K}{220} \right) = 1.25 (1 + 10.4)$$
  
= 1.25 × 11.4 = 14.25V

Since the output terminal produces a voltage of 1.25v, the voltage across the adjustment terminal will produce a voltage given by

14.25V - 1.25V = 13V

Which is the voltage across  $R_2$  and  $R_v$ . Variable resistor 10K pot ( $R_v$ ) in the gain control varies the output voltage between 0.20v - 15.85v.

The capacitor C<sub>3</sub> improves the ripple (and spike) rejection by about 15dB, thereby increasing the rejection factor of the LM317 from 65Db to 80dB. The diode D5 acts as safety diode by allowing current not to flow back to the system.

### 3.0 TEST, ANALYSIS AND OBSERVATION

3.1 TEST AND ANALYSIS

Test and analysis were carried out using the constructed power supply unit to power various loads. The results obtained during the test are tabulated below, where table 1. indicates voltage and current at different conditions. Table 2. explains a load (Rheostat) of 1260hmsand 1A was connected across the power supply, while Table 3 express for load 11 ohms 4A.

$$Load regulation = \frac{\Delta v_o}{v} \times 100$$
(2)  

$$Where \Delta v_o = I_1 \times Z_o = 3 \times 0.008 = 0.024$$

$$Load regulation = \frac{0.024 \times 100}{15} = 0.016 \times 100 = 0.16\%$$

$$Line regulation = \frac{change in output \times 100}{change in input voltage}$$
(3)  

$$Line regulation = \frac{(15.9-15.5) \times 100}{220-180} = \frac{0.4 \times 100}{40} = 0.1\%$$

3.2 OBSERVATION

It was observed that when the power supply unit (PSU) was used to power a load of 11 ohms 4A, the heat of the system increased indicating that load with high current rating would stress the system, while powering 126 Ohms 1A, the heat of the system reduced if using load with low current rating .Figure 4 and 5 shows the characteristic of a stabilized standard power supply voltage. By comparison, the two graphs meet the same standard and their regulation characteristics is the same. Which denote that the constructed stabilize variable power supply met the requirement of a standard power supply unit (SVPSU)

# **4.0. CONCLUSION**

A stabilize variable power supply unit with output voltage ranging from 0.20v - 15.85v, an output current range of 0-3A, power of 45W, output impedance of 0.0080 hms, line regulation of 0.1%, and load regulation of 0.16% has been designed and successfully constructed. This work has been constructed using materials that are relatively cheap when compared to conventional power supply unit of the same output range in the market. It was tested and it met the requirements for a standard power supply unit for a laboratory.

# 5.0 RECOMMENDATION/SOLUTIONS

For further improvement on this work, the following recommendation given below will be advantageous: The current range can be increased so that it would be applicable in powering high power devices in the laboratory. A

voltage protector circuit can be incorporated into the unit to protect the power supply from very low and high mains voltage. A capacitor can be connected in parallel to each of the four power diode, in other to filter out noise.

# Reference

[1] Adejumobi I. A., Olanipekun A. J., Adebisi O. I. & Adeomi A. A.,2012 "Development Of A Multi Ac/Dc Power Supply System For Domestic And Laboratory Use", Vol 12 Issue1/ Ijrras 12.

[2] Aktan O., Sariolu B., Cindemir U., Onur Unlu S., Dunder G., Mutlu S., Yalcinkaya A. D, 201: Cmos Power Supply Unit For Electrically Isolated Micro Scale Application. Pg 747-756.

[3] Amos S .W. 1981: Dictionary Of Electronics, Heinemann Education Books London (H.E.B) Pp.224

[5] Coughlin. R. F. and Daiscod. F. F. 1992: Operational Amplifier And Linear Integrated Circuit (4<sup>th</sup> Edition) Prentile – Hall Of Indian, Private Ltd. New Delhi – 110001.

[6] Filtegerald A. E. Higginbotham. O. E And Grabel. L. A. M. (1988): Basic Electrical Engineering (5<sup>th</sup> Edition) Megraw-Hill Books Company, New York.

[7] Fair Child Groups; 1967: Appliction Engineering Staff Of The S. G. S. Industrial Circuit Handbook. Fair Child Publication.

[8] G. L. Tater; 1976: The Mpc1000 - Super Regulator, Ham Radio, Pg 52-54

[9] Harrison G; 1975: Basic Electronics, Resistor In Circuit, Capacitor In Circuit. The English University Press Ltd Ibadan, Nigeria.

[10] Horowitz. P. And Hill W; 1995: The Art Of Electronics, Cambridge University Press, Campbridge.

[11] Martin Hartley. J. 1990: A Practical Introduction To Electronic Circuits, Cambridge, University Press. Cambridge.

[12] Morris. C. 1992: Electronic Circuit, Design And Application (2<sup>nd</sup> Edition) Mcmillian Education Limited, London.

[13] Olson. H. 1973: Second Generation Ic Voltage Regulators; Ham-Radio Magazine.

Subrahmanyam S. 1982: Experiment In Electronics Mcmillian Education, Toronto Canada.

[14]Seigler D. P; 1973: A Basics Electronics Technology Bruce Co-Operation, Beverly Hills California.

[15] Waterworth G.; 1988: Work Out Electronics. Mcmillian Education Limited, London.

[16] Woolard B. 1984: Practical Electronics (2<sup>nd</sup> Edition) Megraw – Hill Books Company (Uk) And Cambridge University Press, Cambridge.

TABLE 1. Shows voltage and current at unicient conditions	
FULL VOLTAGE (NO LOAD)	15.85V
LEAST VOLTAGE (NO LOAD)	0.20V
CURRENT FLOW	0A
VOLTAGE (FULL LOAD)	15V
CURRENT FLOW	0.12A

# TABLE 1: Shows voltage and current at different conditions

# TABLE 2: V/I for 126 ohms 1A

TADLE 2. V/T 101	120 Units 1A
VOLTAGE (V)	CURRENT (I)
15	0.12
15	0.20
15	0.28
15	0.36
14.9	0.44
14.9	0.52
14.9	0.60
14.8	0.68
14.8	0.76
14.8	0.84
10.0	0.92
10.0	1.00
10.0	1.08
5.0	2.5
2.5	2.7
0	3.0
TABLE 3: V/I for 11ohms 4A.	

# TABLE 3: V/I for 110hms 4A.

VOLTAGE (V)	CURRENT (A)
15	0.12
15	0.18
15	0.24
15	0.30
15	0.36
14.9	0.42
14.9	0.48
14.9	0.54
14.9	0.60
14.8	0.66
14.8	0.72
14.8	0.78
14.8	0.84
14.7	0.90
14.6	0.96
13.8	1.02
12.4	1.20
10.0	1.50
5.0	2.5
2.5	2.7
0	3.0

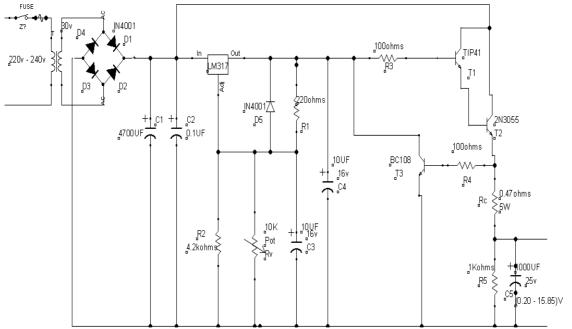


Fig. 1: Circuit diagram of power supply

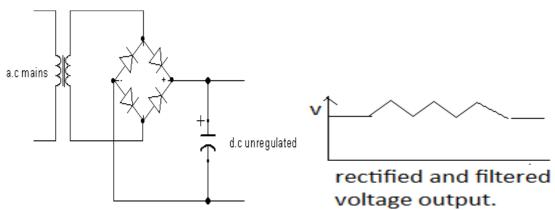


Fig 2: Rectification -Filtration Circuit with its wave form.


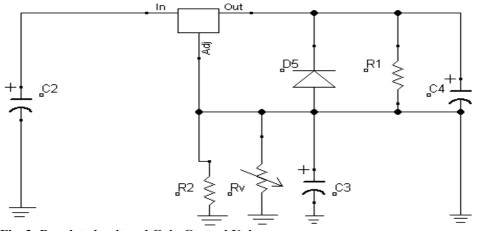


Fig. 3: Regulated unit and Gain Control Unit

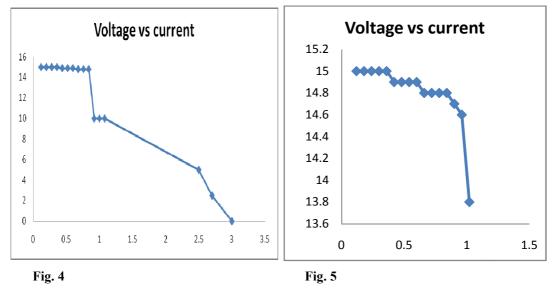

Regulation Characteristics with load of 126  $\Omega$  1A in Figure 4 and load 11  $\Omega$  4A in Figure 5 respectively.

The IISTE is a pioneer in the Open-Access hosting service and academic event management. The aim of the firm is Accelerating Global Knowledge Sharing.

More information about the firm can be found on the homepage: <u>http://www.iiste.org</u>

# CALL FOR JOURNAL PAPERS

There are more than 30 peer-reviewed academic journals hosted under the hosting platform.

**Prospective authors of journals can find the submission instruction on the following page:** <u>http://www.iiste.org/journals/</u> All the journals articles are available online to the readers all over the world without financial, legal, or technical barriers other than those inseparable from gaining access to the internet itself. Paper version of the journals is also available upon request of readers and authors.

# MORE RESOURCES

Book publication information: <u>http://www.iiste.org/book/</u>

# **IISTE Knowledge Sharing Partners**

EBSCO, Index Copernicus, Ulrich's Periodicals Directory, JournalTOCS, PKP Open Archives Harvester, Bielefeld Academic Search Engine, Elektronische Zeitschriftenbibliothek EZB, Open J-Gate, OCLC WorldCat, Universe Digtial Library, NewJour, Google Scholar

